



Progressive Education Society's
Modern College of Arts, Science & Commerce Ganeshkhind, Pune – 16
End Semester Examination: Jan.2023
Faculty: Science and Technology

Program: BSc 09

Semester: I

SET: A

Program (Specific): BSc General

Course Type: CC

Class: FYBSc

Max.Marks: 35

Name of the Course: Basics of Applied Electronics

Course Code: 22-EL111

Time: 2Hr

Paper: I

Instructions to the candidate:

- 1) *There are 4 sections in the question paper. Write each section on separate page.*
- 2) *All Sections are compulsory.*
- 3) *Figures to the right indicate full marks.*
- 4) *Draw a well labelled diagram wherever necessary.*

SECTION: A

Q1) Explain the following

5

- 1) State Kirchhoff's Voltage law
- 2) What is Inductance of Inductor
- 3) State working principle of Battery
- 4) State important specifications of Relay
- 5) What is the function of a Switch

Q2) Answer the following (Solve any 4)

4

- 1) State Maximum Power Transfer Theorem
- 2) Explain Capacitive Reactance
- 3) State Kirchhoff's Current Law
- 4) What is Electronic System
- 5) State function of SIM card in smart phone
- 6) What is Ideal voltage source

SECTION: B

Q3) Answer the following (Attempt any 4) 8

- 1))State any Four important features of Smart phone
- 2))What is CCTV system
- 3)) What is Thermostate
- 4))Expain Tolerance of Resistance
- 5))Write short note on cables
- 6))Write short note on connectors in Electronics equipment

SECTION: C

Q4) Answer the following (Attempt any 4) 8

- 1) Explain Series combination of Inductor
- 2) What is GPS feature in smart phone
- 3) Explain touch screen operation in smart phone
- 4) Fuse is called as safety device Explain
- 5) Explain working of series LCR circuit
- 6) Explain parallel combination of Capacitor

SECTION: D

Q5) Answer the following (Attempt any 2) 10

- 1)Explain Public Address system
- 2)Explain 4 Band colour code system used to indicate the value of Resistors
- 3)State and Explain Superposition Theorem
- 4)State the function of SIM card in smart phone