



Progressive Education Society's  
Modern College of Arts, Science & Commerce Ganeshkhind, Pune – 16  
End Semester Examination: Jan.2023  
Faculty: Science and Technology

Program: BSc

Semester: I

SET: B

Program (Specific): BSc General

Course Type: CC

Class: FYBSc

Max. Marks: 35

Name of the Course: Electronics Devices and Circuits

Course Code: 22\_EL-112

Time: 2Hr

Paper: II

Instructions to the candidate:

- 1) *There are 4 sections in the question paper. Write each section on separate page.*
- 2) *All Sections are compulsory.*
- 3) *Figures to the right indicate full marks.*
- 4) *Draw a well labelled diagram wherever necessary.*

SECTION: A

Q1) Answer the following

5

- 1) Give circuit symbol of Zener diode, P-N diode
- 2) Give circuit symbol of LED, LDR
- 3) Give circuit symbol of photodiode, Photo transistor
- 4) Give circuit symbol of P-N-P and N-P-N transistor
- 5) Give circuit symbol of FET

Q2) Answer the following (Attempt any 4)

4

- 1) Explain the circuit diagram of CE configuration of BJT
- 2) Define Switching transistor
- 3) Draw the circuit diagram of Transistor as a switch
- 4) Draw practice circuit of transistor as amplifier
- 5) Compare Half wave and Full wave rectifier any two points

**6) State and explain operating principle of P-N junction diode in forward bias mode**

**SECTION: B**

**Q3) Answer the following(Attempt any 4) 8**

- 1) State any two applications of LDR**
- 2) Define Breakdown voltage of a P-N diode**
- 3) Define barrier potential in P-N diode**
- 4) Draw I-V characteristic of P-N junction rectifier diode in reverse bias mode**
- 5) Draw circuit diagram to study CB characteristic of transistor**
- 6) Give two applications of optocoupler**

**SECTION: C**

**Q4) Answer the following(Attempt any 2) 8**

- 1) Draw circuit diagram of Bridge rectifier**
- 2) Draw circuit of FET as voltage variable resistance**
- 3) Explain use of diode in mobile charger**
- 4) State any two Regulator IC in 78xx and 79xx series**

**SECTION: D**

**Q5) Answer the following ( Attempt any 2) 10**

- 1) Explain Construction and working of a photodiode**
- 2) Explain with neat circuit diagram working principle of optocoupler.**
- 3) Compare BJT, MOSFET**
- 4) Explain with diagram the effect of forward and reverse bias on barrier potential of rectifying diode**