



**Progressive Education Society's
Modern College of Arts, Science & Commerce Ganeshkhind, Pune – 16
End Semester Examination: Jan.2023
Faculty: Science and Technology**

Semester: I

Program: BScComp05

Program (Specific): B.Sc.(Computer Science)

Class: F.Y. B.Sc. (Comp. Sc.)

Name of the Course: Principles of Digital Electronics

Course Code: 22-ELC-112

Paper: II

SET: A

Course Type: CC

Max. Marks: 35

Time: 2Hr

Instructions to the candidate:

- 1) *There are 4 sections in the question paper. Write each section on separate page.*
- 2) *All Sections are compulsory.*
- 3) *Figures to the right indicate full marks.*
- 4) *Draw a well labelled diagram wherever necessary.*

SECTION: A

Q1) Define

5

- I) Encoder .
- II) Base of a number system. What is the base of (i) decimal number system and (ii) hexadecimal number system.
- III) Propagation delay.
- IV) Weighted code. Give one example.
- V) Define Combinational circuit. Give one example.

Q2) Very short answer questions (Attempt any 4/6)

4

- I) Write the difference between Gray code and BCD code.
- II) Draw logic diagram of half subtractor.
- III) "Multiplexer circuit can be built by using OR-OR combination of logic gate", state whether this statement is true or false.
- IV) Give any 2 uses of De-multiplexer.
- V) Draw the truth table of half adder.
- VI) Write a full form of ASCII code.

SECTION: B

Q3) Short answer questions (Attempt any 2/3)

8

- I) State and verify De-Morgan's 1st and 2nd theorems.
- II) Summarize working of 1:4 de-multiplexers. Draw its logic diagram.
- III) Write a short note on BCD code. Convert $(125)_{10}$ to BCD.

SECTION: C

Q4) Short answer questions (Attempt any 2/3)

8

- I) Explain 2's complement subtraction method. Solve $(57)_{10} - (89)_{10}$ using 2's complement techniques
- II) Write a short note on Universal Gates. Build OR gate using only NAND gates.
- III) Solve the Boolean expression using k-map $\overline{A} \overline{B} \overline{C} + \overline{A} B \overline{C} + A B \overline{C} + \overline{A} \overline{B} C + A \overline{B} \overline{C} + A B C$. Draw the simplified diagram.

SECTION: D

Q5) Attempt any two of the following (2/4)

10

- I) Draw neat logic diagram of 4 bit Universal adder/subtractor. Explain its working.
- II) Solve the following.
 - i) $(111011)_2 = (?)_{10}$ ii) $(376.15)_{10} = (?)_2$
- III) Compare POS and SOP at any 2 point. Convert give expression into its standard POS $(A+B+C+D).(A+B+C).(A+B+D)$
- IV) Discuss the working of decimal to BCD encoder and also draw the logic diagram.
