



Progressive Education Society's
Modern College of Arts, Science & Commerce Ganeshkhind, Pune – 16
End Semester Examination: Jan.2022
Faculty: Science and Technology

Program: B.Sc. Semester: I SET: A
Program (Specific): B.Sc(Computer Science) Course Type: CC
Class: FYBSc(Computer Science) Max.Marks: 35
Name of the Course: Semiconductor Devices and Basic Electronic Systems
Course Code: 22-ELC-111 Time: 2Hr
Paper: I

Instructions to the candidate:

- 1) *There are 4 sections in the question paper. Write each section on separate page.*
- 2) *All Sections are compulsory.*
- 3) *Figures to the right indicate full marks.*
- 4) *Draw a well labelled diagram wherever necessary.*

SECTION: A

Q.1) Define or Explain

[5 Marks]

- I. Intrinsic Semiconductor
- II. Barrier Potential
- III. α of BJT
- IV. Rectification
- V. Resolution of DAC

Q2) Answer the following (Attempt any 4 out of 6)

[4 Marks]

- I. Draw the symbol of NPN and PNP transistor
- II. What is the role of filter circuit in Power Supply ?
- III. What is an opto-coupler?
- IV. Which type of ADC is the fastest ADC?
- V. List different configurations of BJT.
- VI. For a BJT, $\alpha = 0.96$, $I_E = 4\text{mA}$. Calculate I_C

SECTION: B

Q3) Answer in brief (Attempt any 2 out of 3)

[8 Marks]

- I. Illustrate the working of Bridge rectifier with neat diagram.**
- II. What do you mean by UPS? Describe the working of On-Line UPS.**
- III. Summarize the working of successive approximation ADC with its block diagram.**

SECTION: C

Q4) Answer in brief (Attempt any 2 out of 3)

[8 Marks]

- I. Draw the block diagram of regulated power supply and explain the role of each block in it.**
- II. Summarize the working of reverse biased PN junction diode along with its I-V characteristics**
- III. Explain the working of Wein Bridge Oscillator.**

SECTION: D

Q5) Answer in details (Attempt any 2 out of 4)

[10 Marks]

- I. What are voltage regulators? State different types of voltage regulators.**
- II. What is multivibrator ? Explain the working of astable multivibrator using IC 555.**
- III. For a 4 bit R-2R ladder DAC ,determine the following**
 - a) The weight assigned to LSB**
 - b) The change in the output voltage due to change in LSB.**
 - c) Analog output voltage for digital input of 1100 (Assume Logic '0' = 0V and Logic '1' =10 V)**
- IV. Compare BJT and MOSFET .**
