



Progressive Education Society's
Modern College of Arts, Science & Commerce Ganeshkhind, Pune - 16 (Autonomous)
End Semester Examination: 2023-24
Faculty: Science and Technology

Program: B.Sc. Code (Gen03)
Program (Specific): General B.Sc.
Class: S.Y.BSc (Gen)
Name of the Course: Electronics
Course Code: 23-PHY-232(A)
Paper: II

Semester: III

SET: B
Course Type: Core course
Max. Marks: 35

Time: 2Hr

Instructions to the candidate:

- 1) There are 4 sections in the question paper. Write each section on separate page.
- 2) All Sections are compulsory.
- 3) Figures to the right indicate full marks.
- 4) Draw a well labelled diagram wherever necessary.

SECTION: A

Q1) Answer the following (any 5 out of 7)

5


- i) Draw circuit for voltage shunt feedback.
- ii) Write two important applications of Unijunction Transistor (UJT).
- iii) What is transistor?
- iv) State relation between α and β in context with transistor.
- v) State Thevenin's theorem.
- vi) Find one's complement of 010011001.
- vii) Convert $(1111)_2$ to decimal.

SECTION: B


Q2) Answer the following (any 5 out of 7)

10

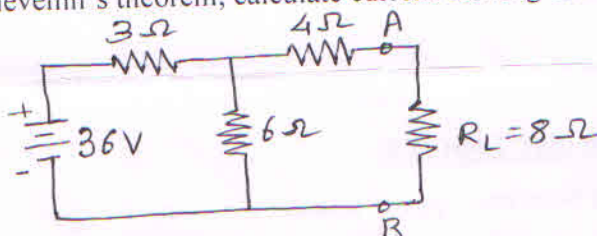
- i) Using Thevenin's theorem, calculate current flowing through R_L in following circuit.



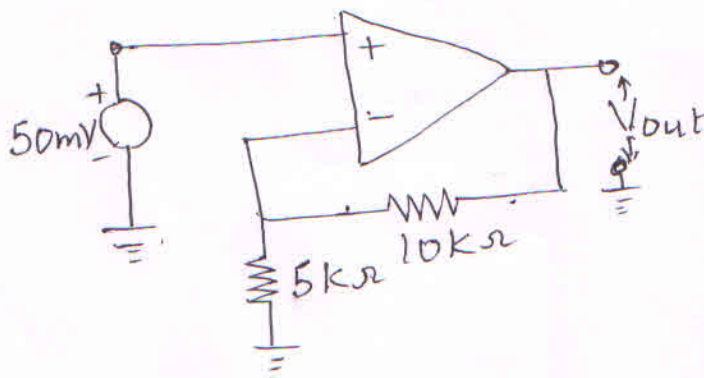- ii) What will be the output V_o for the following circuit?



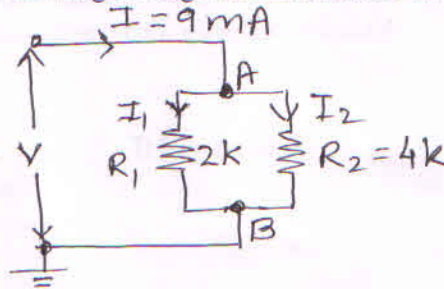- iii) Find the current flowing through each resistance in the following circuit.



- iv) What will be the frequency of oscillation when a combination of three resistances each value of 100Ω and three capacitors each of value $0.1\mu F$ are connected in phase shift oscillator using IC 741?
- v) With the help of a neat diagram, explain the concept of virtual ground.
- vi) Write a short note on Ex-NOR gate.
- vii) Convert $(01011111011)_2$ to hexadecimal.

SECTION: C

Q3) Answer the following (any 4 out of 6)

12

- Add the binary numbers.
a) 1011 and 1100 b) 0101 and 1111
- Convert $(3A9)_{16}$ to decimal.
- What is an oscillator? Give types of oscillators.
- Derive the equation for the gain of inverting Op-amp.
- Explain biasing of common emitter transistor using base resistor method.
- Explain the construction of Unijunction Transistor (UJT).

SECTION: D

Q4) Answer the following (any 2 out of 4)

8

- State and prove Maximum power transfer theorem.
- Explain the use of transistor as a switch with circuit diagram.
- Explain op-amp as subtractor with circuit diagram.
- State and prove De-Morgan's theorem.

-----X-----