



Progressive Education Society's
Modern College of Arts, Science & Commerce Ganeshkhind, Pune – 16
(Autonomous)
End Semester Examination: OCT / NOV 2024
Faculty: Science and Technology

Program: B.Sc. Code (Gen 03)	Semester: V	SET: A
Program (Specific): General B.Sc.		Course Type: Core
Class: T.Y.B.Sc. (Gen)		Max. Marks: 35
Name of the Course: Basics of Electrical Wiring		
Course Code: 24-PHY-3511		Time: 2Hr
Paper: XI		

Instructions to the candidate:

- 1) *There are 4 sections in the question paper. Write each section on separate page.*
- 2) *All Sections are compulsory.*
- 3) *Figures to the right indicate full marks.*
- 4) *Draw a neat labelled diagram wherever necessary.*

SECTION: A

Q1) Define or Explain the following. (5 Marks)

- i) State Fleming's left-hand rule.
- ii) What is the self-inductance of a coil?
- iii) State Norton's theorem.
- iv) State Kirchhoff's current law.
- v) Write the names of any four components used in electric wiring.

Q2) Answer the following questions. (Attempt any four) (4 Marks)

- i) State importance of earthing related to electrical wiring systems.
- ii) What are open and closed circuits?
- iii) State Lenz's law.
- iv) State the use of a fuse wire.
- v) Write names of any two types of insulating material.
- vi) What is the magnitude of impedance and the phase angle in a series RLC circuit?

SECTION: B

Q3) Answer the following.

(Attempt any four)

(8 Marks)

- i) What is the importance of wiring diagrams and symbols?
- ii) A practical resonant circuit has an inductor of 0.24 H and a capacitor of 3 μF , the capacitor can be assumed to be lossless. The resistance of the inductor is 150 Ω , find the resonant frequency and quality factor.
- iii) Explain the use of MCB in electric wiring system.
- iv) Differentiate between a constant current and constant voltage source.
- v) Explain working of a half wave rectifier.
- vi) With the help of a neat diagram show how live, neutral and earth wires are connected in a three pin socket. What is the function of these wires?

SECTION: C

Q4) Answer the following.

(Attempt any two)

(8 Marks)

- i) With the help of a neat, labelled diagram, explain working of a voltage divider circuit.
- ii) Define time constant? Explain time constant in case of series R-C circuit.
- iii) Explain the use of following tools used in carrying out electrical wiring installations.
1. Screw driver 2. Tester 3. Nose plier 4. Cutter
- iv) With the help of a neat diagram explain mutual inductance of a coil.

SECTION: D

Q5) Attempt any two of the following.

(10 Marks)

- i) State Thevenin theorem. How to thevenize a circuit.
- ii) With the help of a neat diagram, explain the use of Zener diode as a voltage regulator.
- iii) Write a note on types of cables.
- iv) Explain Wye and Delta inter connection of three phase systems.