



Progressive Education Society's
Modern College of Arts, Science & Commerce Ganeshkhind, Pune – 16
(Autonomous)
End Semester Examination: MAR / APR 2025
Faculty: Science and Technology

Program: B.Sc. (Gen03)
Program (Specific): General B.Sc.
Class: T.Y.B.Sc.
Name of the Course: Electronics
Course Code: 24-PHY-365
Paper: V

Semester: VI

SET: A
Course Type: DSC
Max. Marks: 35

Time: 2Hr

Instructions to the candidate:

- 1) *All Questions are compulsory.*
- 2) *Figures to the right indicate full marks.*
- 3) *Draw a well labeled diagram wherever necessary.*
- 4) *Use of a scientific calculator and log table is allowed.*

Q1) Answer the following:

5

- i) Draw opto-coupler circuit.
- ii) Define duty cycle.
- iii) Draw symbols of N and P-channel JFET.
- iv) Draw circuit diagram of integrator.
- v) What is meant by monostable multivibrator?

Q2) Answer the following (Any four):

4


- i) What do you mean by SOP?
- ii) Draw a circuit of half adder.
- iii) What do you mean by multiplexer?
- iv) What is shift register?
- v) State unit of trans-conductance.
- vi) Draw logic diagram of R-S flip-flop with NAND gates.

Q3) Answer the following (Any four):

8

- i) When a reverse gate voltage of 20 V is applied to a FET, the gate current is $10^{-3} \mu\text{A}$. Find the resistance between gate and source.

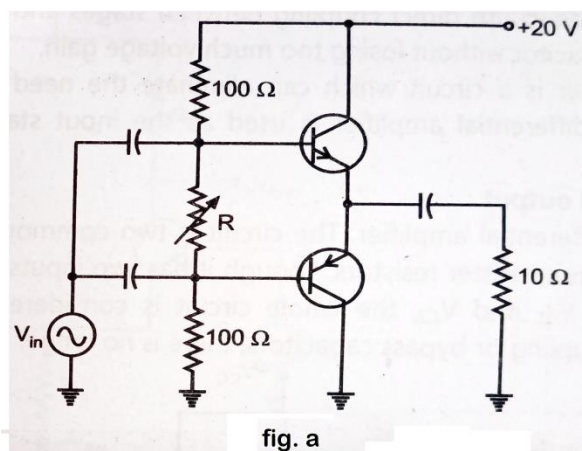- ii) A JFET has $V_p = 5V$ and $I_{DSS} = 100 \text{ mA}$. What is ohmic resistance? What is the gate source cut-off voltage?
- iii) The adjustable resistor of fig. (a) sets both emitter diodes on the verge of conduction. What is the maximum transistor power dissipation and the maximum output power?



- iv) A 5-bit asynchronous counter begins with 00000 state. What will be the state of a counter after 80 input pulses?
- v) Convert $Y = AB + \overline{A}BC$ into standard SOP form.
- vi) Draw circuit diagram of astable multivibrator.

Q4) Answer the following (Any two):

8

- Explain seven segment display with circuit diagram.
- Explain the working of class B push-pull emitter follower.
- Draw circuit diagram for differentiator using op-amp. Derive the expression for it.
- Determine the frequency of oscillation for the astable multivibrator using IC555. Given data is $R_A = R_B = 10k\Omega$ and $C = 0.01\mu F$.

Q5) Answer the following (Any two):

10

- Using K- map technique minimise the following logical expression in the SOP form

$$Y = \overline{A} B \overline{C} \overline{D} + A B \overline{C} \overline{D} + \overline{A} B \overline{C} D + A B \overline{C} D.$$
- Draw a circuit diagram of a 4-bit SIPO shift register. Explain its working.
- Explain the working principle of JFET.
- Explain working of a 4-bit synchronous counter using a diagram.

-----X-----