



Total No. of Questions: 4/18

Total No. of Pages:

**FIRST YEAR (FYBSc)**  
**EL 12102: Fundamentals of Digital Electronics**  
**(Semester II)**

**Program: Bsc**

**Credits: 2**

**Program Specific: FYBSC GENERAL Electronics**

**Time: 2 Hours**

**Course Type: ESE**

**Max. Marks: 30**

**Paper: Fundamentals of Digital Electronics**

**SET: A**

**Instructions to the candidate:**

- 1) All questions are compulsory.
- 2) Figures to the right indicate full marks.
- 3) Draw a well labelled diagram wherever necessary.

**Q1) Answer the following**

**[5 X 1= 5]**

- a) Draw the Logic diagram of OR gate using NAND gate
- b) Draw the block diagram of Half adder
- c) Draw JK FlipFlop using NAND Gate
- d) Explain positive and Negative logic
- e) Write DeMorgans Theorem

**Q2) Answer the following (Attempt any 5/7)**

**[5 X 2 =10]**

- a) Define Encoder
- b) Define Decoder
- c) Draw D Flipflop and T Flipflop
- d) Define Multiplexer
- e) Define Demultiplexer
- f) Write 1,s compliment of( 110011)
- g) Write 2,s compliment of (1110011)

**Q3) Answer the following (Attempt any 2/4 [2 X 5 = 10]**

- a) Convert Hexadecimal (B7) number into decimal number
- b) Subtract binary number (1010) from( 1111)
- c) Draw R<sub>2</sub>R DAC. (Digital to Analog convertor
- d) Explain in short data converter

**Q4) Answer the following (Attempt any 1/2)**

**[5 X 1 = 5]**

- a) Convert the expression  $Y=AB+AC+BC$  in standard SOP form
- b) Define combinational and sequential Logic circuits with examples.

\*\*\*\*\*